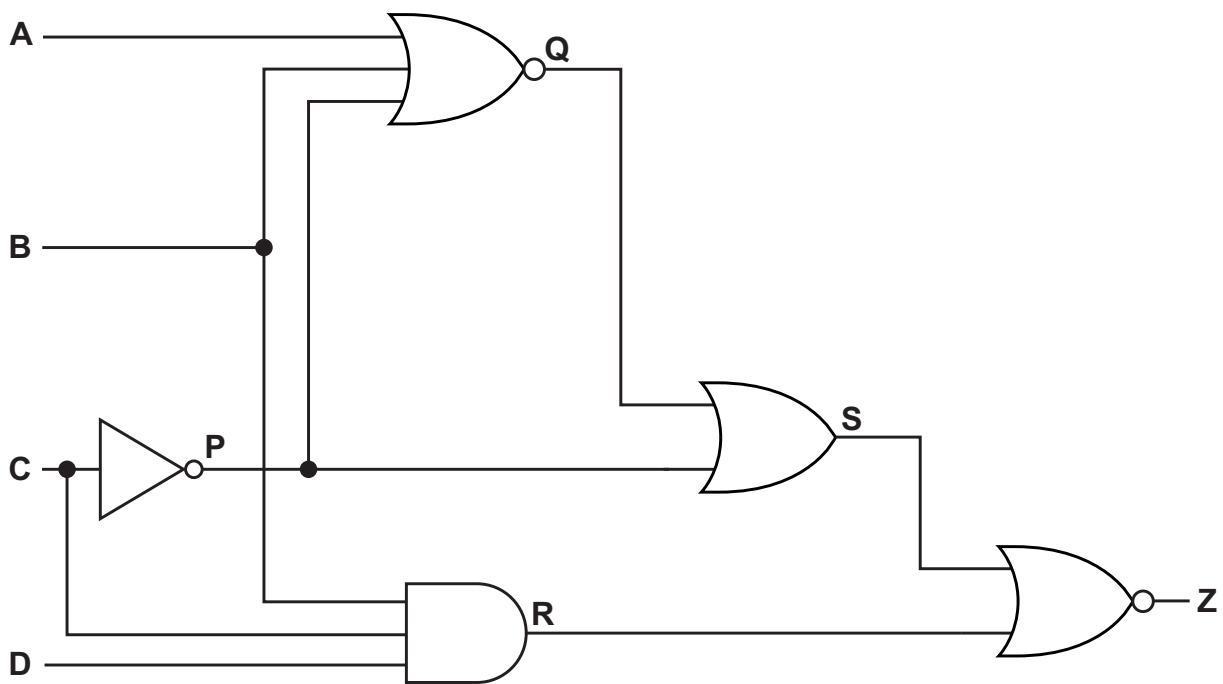


7 The diagram shows a logic circuit.



(a) Complete the truth table for the given logic circuit. Show your working.

				Working space				
A	B	C	D	P	Q	R	S	Z
0	0	0	0					
0	0	0	1					
0	0	1	0					
0	0	1	1					
0	1	0	0					
0	1	0	1					
0	1	1	0					
0	1	1	1					
1	0	0	0					
1	0	0	1					
1	0	1	0					
1	0	1	1					
1	1	0	0					
1	1	0	1					
1	1	1	0					
1	1	1	1					

[3]

(b) Write the Boolean logic expression that corresponds to the given logic circuit as the sum-of-products.

Z = .....  
 ..... [1]

(c) Use Boolean algebra including De Morgan's laws to simplify the following expression. Show all working.

$$\overline{(A + B)} \cdot \overline{(A \cdot B + B \cdot C)}$$

Working .....

.....

.....

.....

.....

.....

.....

.....

Simplified expression .....

.....

[4]