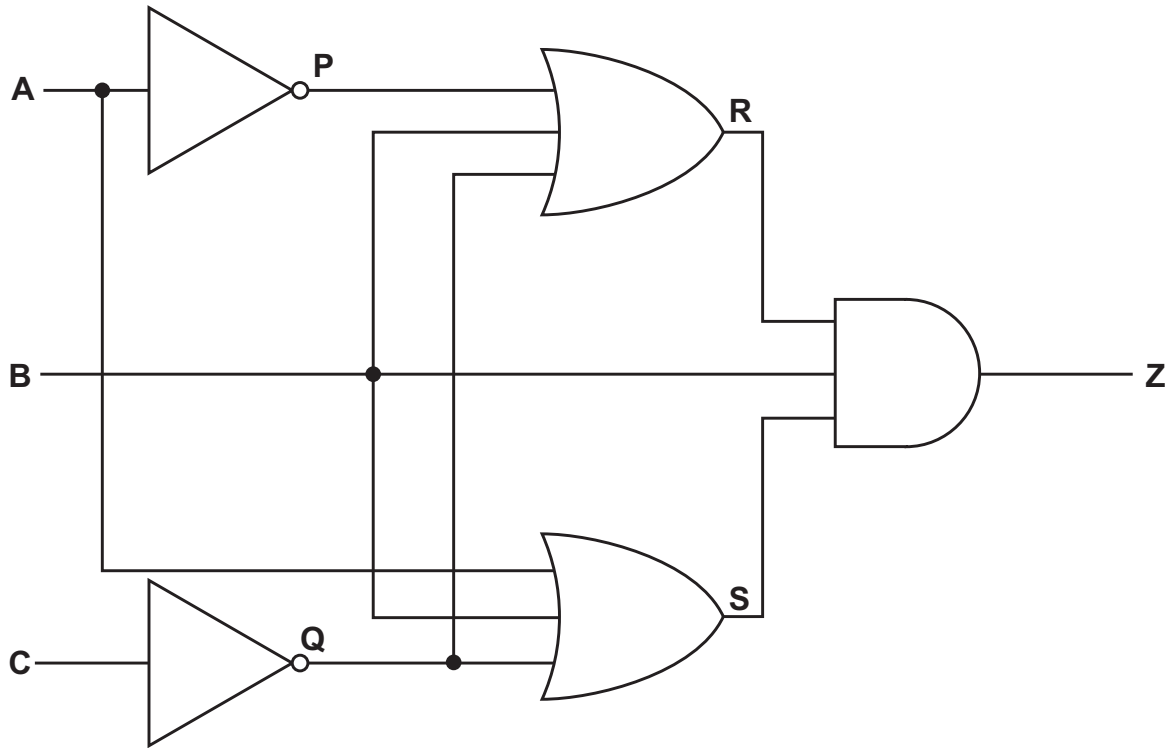


6 (a) The diagram shows a logic circuit.



Complete the truth table for the given logic circuit.  
Show your working.

			Working space				
A	B	C	P	Q	R	S	Z
0	0	0					
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

[3]

(iii) Write the Boolean expression from your answer to part **b(ii)** as a simplified sum-of-products. Do **not** carry out any further simplification.

.....

..... [2]