
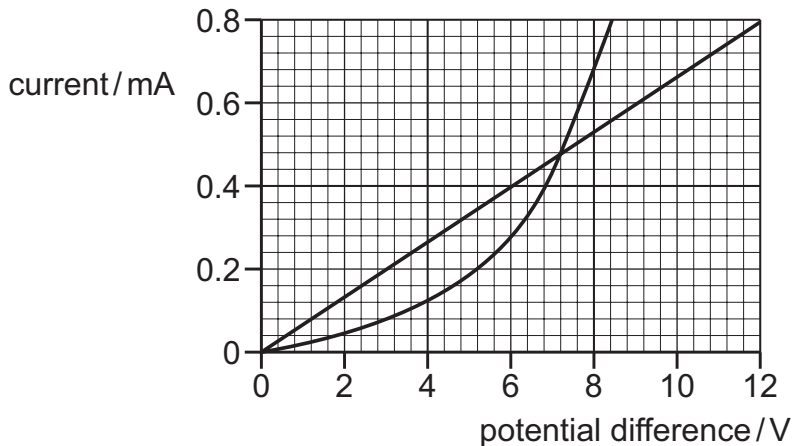


35 The diagram shows a circuit containing a thermistor, a fixed resistor and a battery.

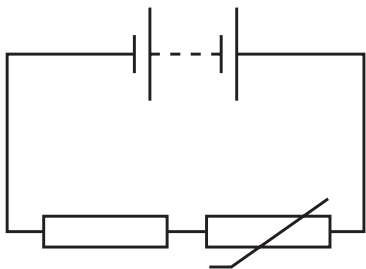The graph shows the I - V characteristics of both components.



The battery has an e.m.f. of 12V and negligible internal resistance.

What is the current in the fixed resistor?

- A** 0.36 mA **B** 0.40 mA **C** 0.48 mA **D** 0.80 mA