

29 The resistance of a lamp is $10\ \Omega$ and the potential difference across it is $6.0\ \text{V}$.

How many electrons pass through the lamp in a time of 24 hours?

A 5.2×10^4

B 9.0×10^{19}

C 5.4×10^{21}

D 3.2×10^{23}