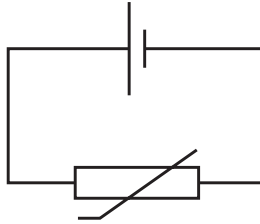


32 A thermistor is connected to a cell with negligible internal resistance.



Which graph shows the variation with temperature of power, P , dissipated in the thermistor?

