

34 A cell of electromotive force (e.m.f.) E delivers a charge Q to an external circuit.

Which statement is correct?

A The energy dissipated in the external circuit is EQ .

B The energy dissipated within the cell is EQ .

C The external resistance is EQ .

D The total energy dissipated in the cell and the external circuit is EQ .