

31 There is a potential difference V across a resistor of resistance R . The current in the resistor is I .

Which equation gives the power P dissipated by the resistor?

A $P = V^2 I$ **B** $P = \frac{V^2}{I}$ **C** $P = V^2 R$ **D** $P = \frac{V^2}{R}$