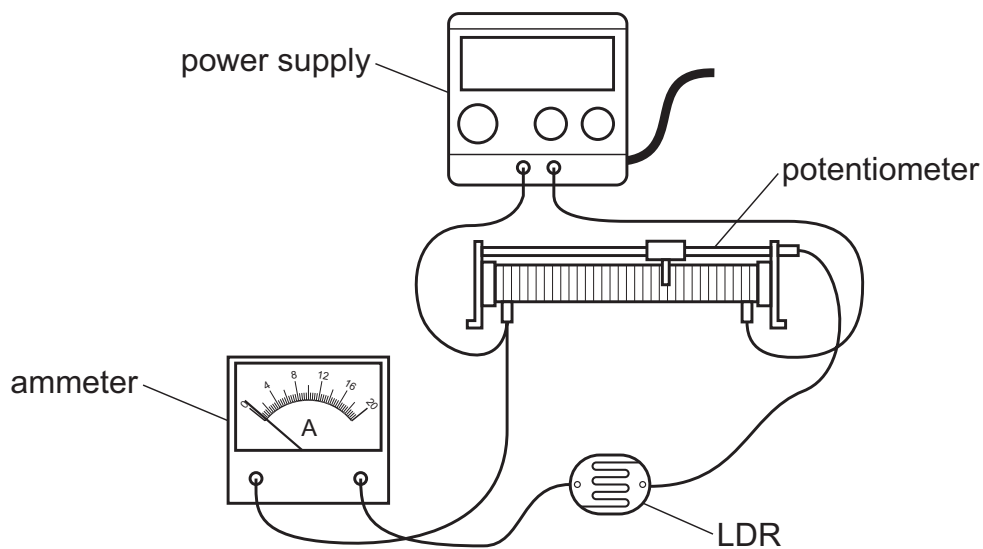


33 The diagram shows an electrical circuit containing a light-dependent resistor (LDR).



What is the circuit diagram for this circuit?

