

2 In this experiment, you will investigate the resistance of a light-dependent resistor (LDR) using the light from a light-emitting diode (LED).

- (a) (i) • Using the LED, set up the circuit shown in Fig. 2.1.

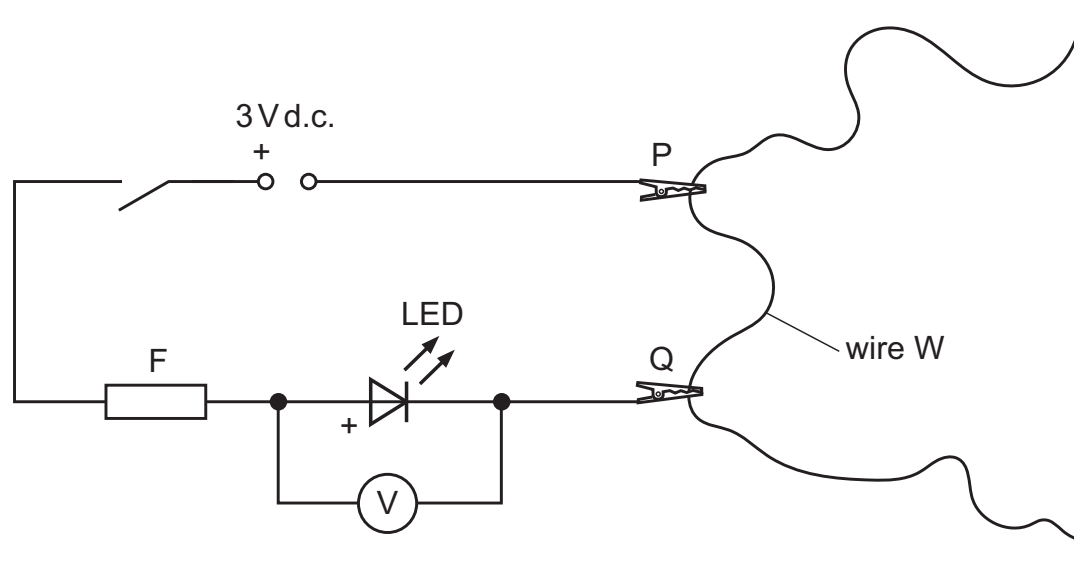


Fig. 2.1

- Ensure that the positive terminal of the power supply and the positive terminal of the LED are connected as shown in Fig. 2.1.
- P and Q are crocodile clips. Position P and Q so that there is approximately 10 cm of wire W between P and Q.
- Close the switch. The LED should light.
- Open the switch.
- Using the LDR and ohmmeter, set up a second circuit as shown in Fig. 2.2.

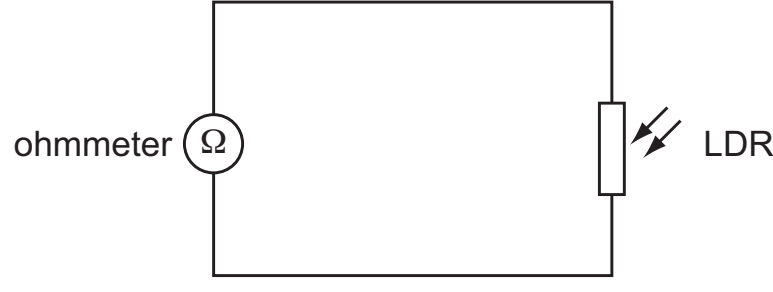


Fig. 2.2

- Arrange the apparatus as shown in Fig. 2.3.

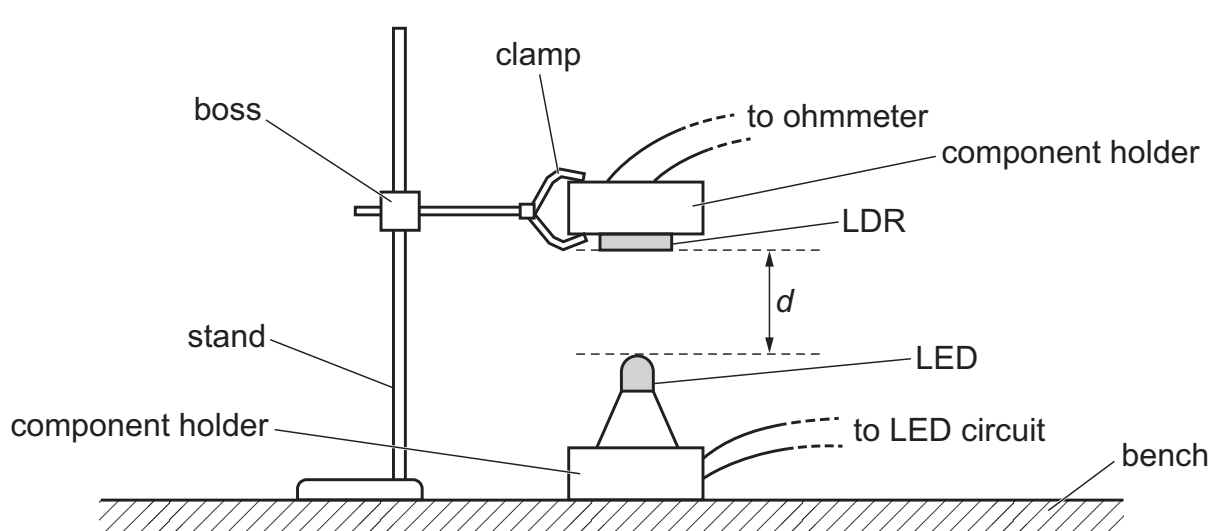


Fig. 2.3 (not to scale)

- The distance between the top of the LED and the surface of the LDR is d . Adjust the position of the LDR so that d is approximately 0.03 m.
- Measure and record d .

$d = \dots\dots\dots$ m [2]

- (ii) Estimate the percentage uncertainty in your value of d . Show your working.

percentage uncertainty = $\dots\dots\dots$ % [1]

- (b) • The length of wire W between P and Q is L .

Measure and record L .

$L = \dots\dots\dots$

- Close the switch.
- The potential difference V across the LED is given by the voltmeter. The resistance R of the LDR is given by the ohmmeter.

Measure and record V and R .

$V = \dots\dots\dots$

$R = \dots\dots\dots$

- Open the switch. [2]

- (c) • Change the length of wire W between P and Q so that L is approximately 90 cm.

- Repeat (b).

$L = \dots\dots\dots$

$V = \dots\dots\dots$

$R = \dots\dots\dots$ [3]

- (d) It is suggested that the relationship between V , d and R is

$$V = \frac{Zd}{R} + k$$

where Z has the value $1.00 \times 10^3 \text{ V}\Omega\text{m}^{-1}$ and k is a constant.

- (i) Using your data, calculate **two** values of k .

first value of $k = \dots\dots\dots$

second value of $k = \dots\dots\dots$ [1]

- (ii) Justify the number of significant figures that you have given for your values of k .

$\dots\dots\dots$
 $\dots\dots\dots$
 $\dots\dots\dots$ [1]

- (e) It is suggested that the percentage uncertainty in the values of k is 5%.

Using this uncertainty, explain whether your results support the relationship in (d).

$\dots\dots\dots$
 $\dots\dots\dots$
 $\dots\dots\dots$
 $\dots\dots\dots$ [1]

- (f) It is suggested that

$$k = \frac{hc}{e\lambda}$$

where h is $6.63 \times 10^{-34} \text{ Js}$,
 c is $3.00 \times 10^8 \text{ ms}^{-1}$,
 e is $1.60 \times 10^{-19} \text{ C}$ and
 λ is the wavelength of the light emitted by the LED.

Use your second value of k to determine λ .

$\lambda = \dots\dots\dots$ m [1]

- (g) (i) Describe **four** sources of uncertainty or limitations of the procedure for this experiment.

For any uncertainties in measurement that you describe, you should state the quantity being measured and a reason for the uncertainty.

- $\dots\dots\dots$
 - $\dots\dots\dots$
 - $\dots\dots\dots$
 - $\dots\dots\dots$
- $\dots\dots\dots$ [4]

- (ii) Describe **four** improvements that could be made to this experiment. You may suggest the use of other apparatus or different procedures.

- $\dots\dots\dots$
 - $\dots\dots\dots$
 - $\dots\dots\dots$
 - $\dots\dots\dots$
- $\dots\dots\dots$ [4]