

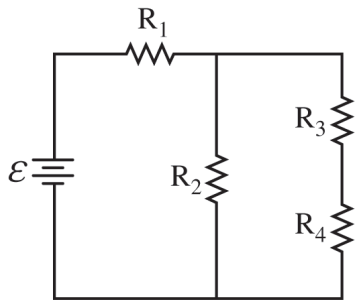


Figure 1

3. (12 points, suggested time 25 minutes)

A circuit consists of an ideal battery of emf $\mathcal{E}$ and four identical resistors R_1 , R_2 , R_3 , and R_4 , each of resistance R , as shown in Figure 1.

- (a) For parts (a)(i) and (a)(ii), express your answers in terms of numerical values, $\mathcal{E}$, and R only.
- i. **Derive** an expression for the current I_1 in Resistor R_1 .

- ii. **Derive** an expression for the current I_3 in Resistor R_3 .

GO ON TO THE NEXT PAGE.

Continue your response to **QUESTION 3** on this page.

- (b) The partially completed bar chart in Figure 2 shows a bar that represents the absolute value $|\Delta V|$ of the potential difference across the ideal battery.
- In Figure 2, **draw** a bar to represent $|\Delta V|$ across each resistor, relative to the emf $\mathcal{E}$ of the ideal battery.
 - The height of each bar should be proportional to the value of $|\Delta V|$ represented by that bar. If $|\Delta V|$ is zero, write a “0” in that column.

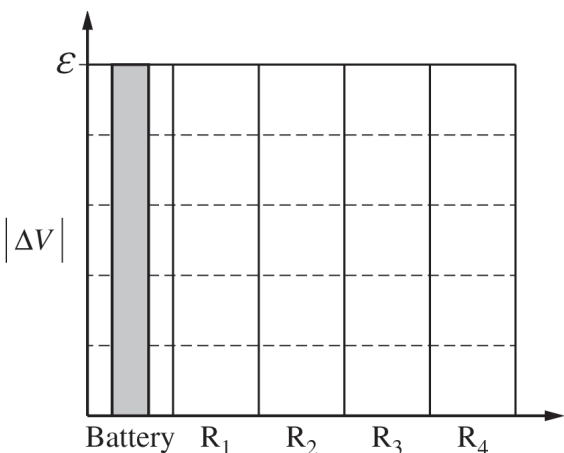


Figure 2

A student claims that the rate at which energy is dissipated (power) by the circuit can be expressed as $P = \frac{3\mathcal{E}^2}{5R}$.

- (c) **State** whether the expression for P is correct or incorrect. **Justify** your answer by referring to the derivations from part (a) or the bar chart from part (b).

GO ON TO THE NEXT PAGE.

Continue your response to **QUESTION 3** on this page.

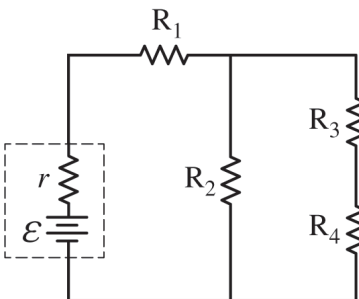


Figure 3

When the ideal battery is connected in the original circuit, the rate at which energy is dissipated by Resistor R_1 is P_{original} . The ideal battery is now replaced with a nonideal battery of emf $\mathcal{E}$ and internal resistance r to form the new circuit shown in Figure 3. The rate at which energy is dissipated by Resistor R_1 in the new circuit is P_{new} .

- (d) **Indicate** whether P_{new} is greater than, less than, or equal to P_{original} .

_____ $P_{\text{new}} > P_{\text{original}}$ _____ $P_{\text{new}} < P_{\text{original}}$ _____ $P_{\text{new}} = P_{\text{original}}$

Briefly **justify** your answer.

GO ON TO THE NEXT PAGE.