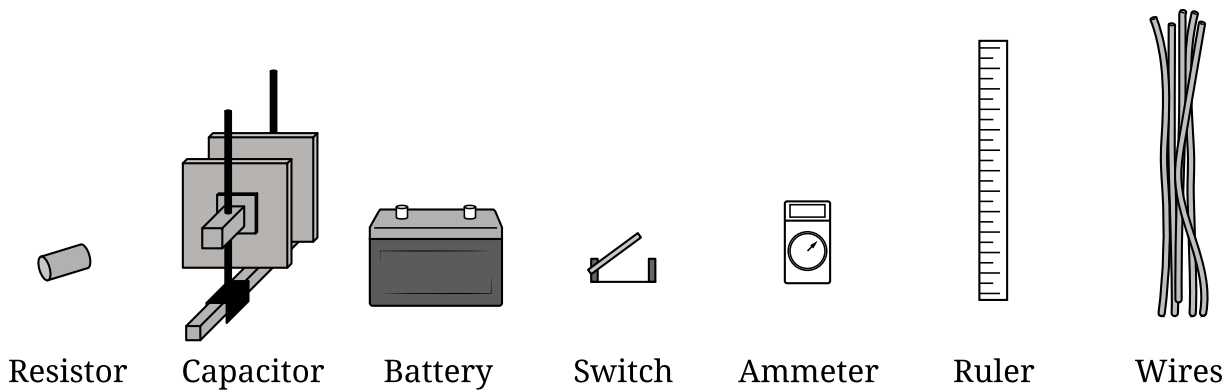


Question 3

3. In Experiment 1, a student is given a resistor of unknown resistance and an air-filled parallel-plate capacitor of unknown capacitance. The student is asked to predict the expected time constant τ of a circuit if these two circuit elements were connected in series with a battery. The student has access to a battery of known emf, a switch, an ammeter, a ruler, and wires, as shown in Figure 1. The plates of the capacitor are square, and the separation between the plates is small compared to the dimensions of the plates. The capacitor is initially uncharged. Assume that the dielectric constant of air is 1.

Figure 1



Note: Figure not drawn to scale.

- A. **Describe** a procedure for collecting data that would allow the student to determine the expected time constant τ . In your description, include the measurements to be made. Include any steps necessary to reduce experimental uncertainty.
- B. **Describe** how the collected data could be analyzed to determine τ . Include references to appropriate equations and to relationships between measured and known quantities.

AP Physics 2 Release 2020-2025 Free Response Questions

C. In Experiment 2, the student is asked to determine the capacitance C of a new parallel-plate capacitor. For each trial, the absolute value $|\Delta V|$ of the potential difference across the capacitor is varied and the charge q stored on one plate of the fully charged capacitor is measured. Table 1 contains the data collected.


Table 1

$ \Delta V $ (V)	q ($\times 10^{-10}$ C)
3.0	2.4
5.0	4.2
7.2	5.6
8.0	6.6
10.0	8.0

- i. **Indicate** two quantities, either measured quantities from Table 1 or additional calculated quantities, that could be graphed to produce a straight line that could be used to determine C .
- Vertical axis: _____ Horizontal axis: _____

AP Physics 2 Release 2020-2025 Free Response Questions

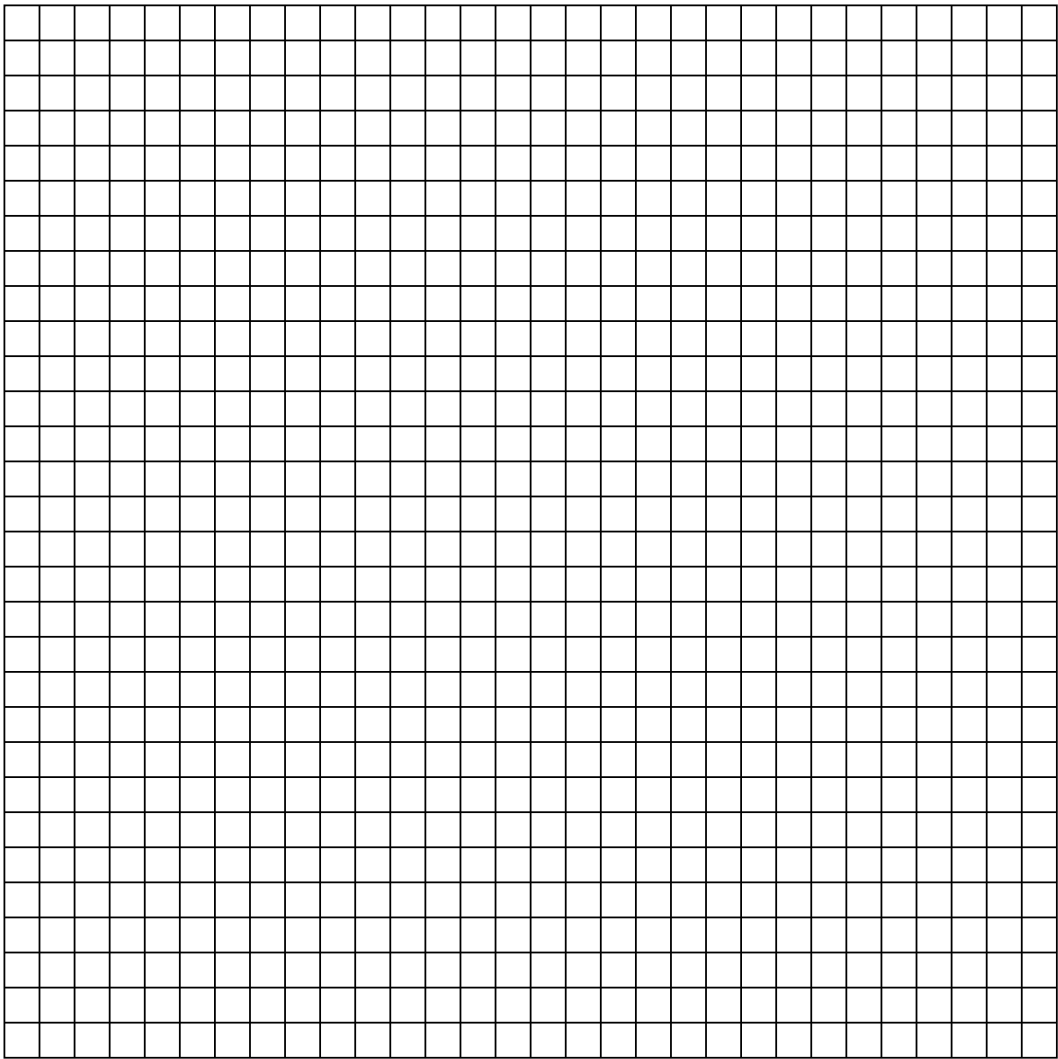- ii. On the grid provided, create a graph of the quantities indicated in part C (i).
- Use Table 2 to record the measured or calculated quantities that you will plot.
 - Clearly **label** the axes, including units as appropriate.
 - Plot** the points you recorded in Table 2.



- iii. **Draw** a best-fit line for the data graphed in part C (ii).
- D. Using the best-fit line that you drew in part C (iii), **calculate** an experimental value for capacitance C .