

Figure 1

2. The circuit shown above is constructed with two 6.0 V batteries and three resistors with the values shown. The currents I_1 , I_2 , and I_3 in each branch of the circuit are indicated.

- (a)
- Using Kirchhoff's rules, write, but DO NOT SOLVE, equations that can be used to solve for the current in each resistor.
 - Calculate the current in the $200\ \Omega$ resistor.
 - Calculate the power dissipated by the $200\ \Omega$ resistor.

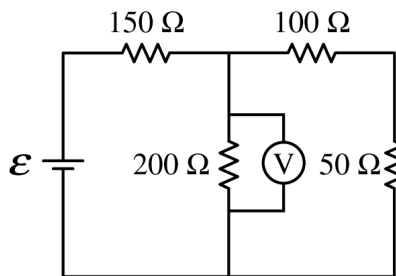



Figure 2

The two 6.0 V batteries are replaced with a battery with voltage $\mathcal{E}$ and a resistor of resistance $50\ \Omega$, as shown above. The voltmeter V shows that the voltage across the $200\ \Omega$ resistor is 4.4 V.

- (b) Calculate the current through the $50\ \Omega$ resistor.
- (c) Calculate the voltage $\mathcal{E}$ of the battery.

(d)

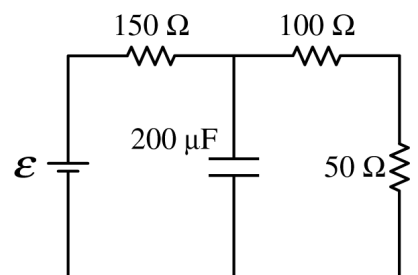- i. The $200\ \Omega$ resistor in the circuit in Figure 2 is replaced with a $200\ \mu\text{F}$ capacitor, as shown on the right, and the circuit is allowed to reach steady state. Calculate the current through the $50\ \Omega$ resistor.



- ii. The $200\ \Omega$ resistor in the circuit in Figure 2 is replaced with an ideal 50 mH inductor, as shown on the right, and the circuit is allowed to reach steady state. Is the current in the $50\ \Omega$ resistor greater than, less than, or equal to the current calculated in part (b) ?

____ Greater than ____ Less than ____ Equal to

Justify your answer.

