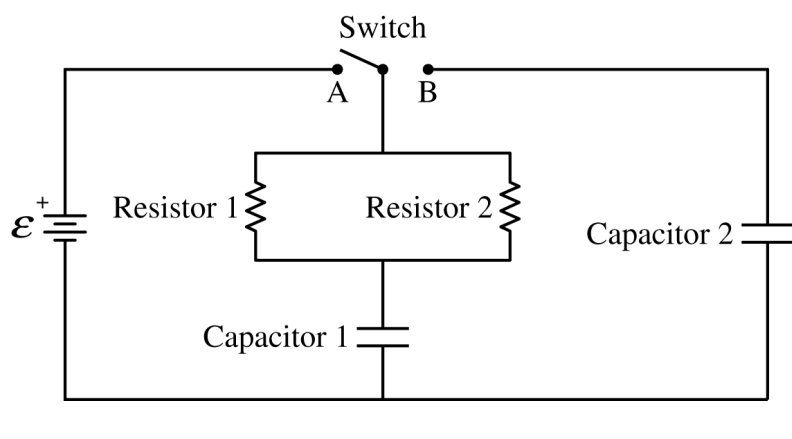




The circuit shown consists of a battery of emf  $\mathcal{E}$ , resistors 1 and 2 each with resistance  $R$ , capacitors 1 and 2 with capacitances  $C$  and  $2C$ , respectively, and a switch. The switch is initially open and both capacitors are uncharged.


At time  $t = 0$ , the switch is closed to Position A.

- (a) Write, but do NOT solve, a differential equation that can be used to determine the charge  $Q$  on the positive plate of Capacitor 1 as a function of time  $t$  after the switch is closed to Position A. Express your answer in terms of  $\mathcal{E}$ ,  $R$ ,  $C$ ,  $Q$ ,  $t$ , and fundamental constants, as appropriate.

**GO ON TO THE NEXT PAGE.**

Continue your response to **QUESTION 3** on this page.

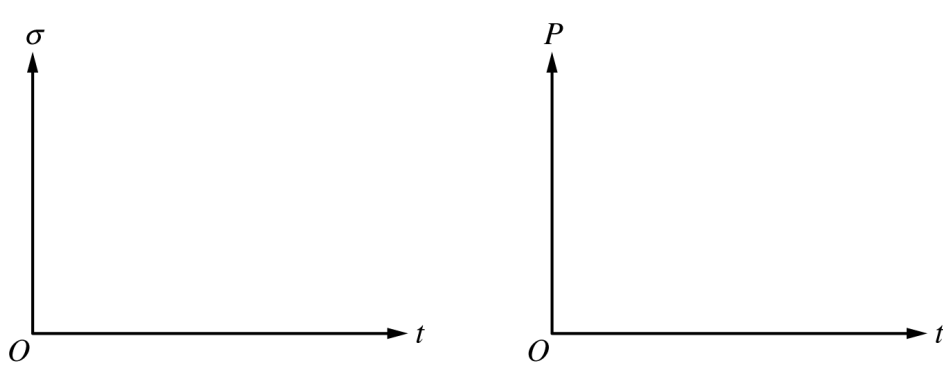- (b) On the axes shown, sketch graphs of the surface charge density  $\sigma$  on the positive plate of Capacitor 1 and the total power  $P$  dissipated by the resistors as functions of time  $t$  from time  $t = 0$  until steady-state conditions are nearly reached.



A long time after the switch is closed to Position A, the charge on the positive plate of Capacitor 1 is  $Q_0$  and Capacitor 2 is uncharged.

- (c) At time  $t_1$ , the switch is closed to Position B.
- Immediately after time  $t_1$ , is the direction of the current in the switch directed toward the left, directed toward the right, or is there no current? Briefly justify your answer.
  - Determine an expression for the total charge on the positive plate of Capacitor 2 a long time after  $t_1$ . Express your answer in terms of  $Q_0$  and fundamental constants, as appropriate.

**GO ON TO THE NEXT PAGE.**

Continue your response to **QUESTION 3** on this page.

- Derive an expression for the total energy  $E_R$  dissipated by resistors 1 and 2 from immediately after time  $t_1$  until new steady-state conditions have been reached. Express your answer in terms of  $C$ ,  $Q_0$ , and fundamental constants, as appropriate.

With the switch still closed to Position B, the parallel plates of Capacitor 2 are moved so that the separation distance increases by a factor of 2.

- (d) Determine the ratio  $\frac{U_2}{U_1}$  of the energy  $U_2$  stored in Capacitor 2 to the energy  $U_1$  stored in Capacitor 1 a long time after the plates of Capacitor 2 have been moved. Briefly justify your answer.

**GO ON TO THE NEXT PAGE.**

Continue your response to **QUESTION 3** on this page.

With the capacitors still charged as in part (d), the switch is now closed to Position A.

- (e) Express your answers to part (e)(i) and part (e)(ii) in terms of  $R$ ,  $C$ ,  $Q_0$ , and fundamental constants, as appropriate.
- Derive an expression for the current  $I_0$  from the battery immediately after the switch is closed to Position A.
  - Determine the current  $I_\infty$  from the battery a long time after the switch is closed to Position A.

**GO ON TO THE NEXT PAGE.**

**STOP**

**END OF EXAM**