

2 **Four** logic functions and **five** standard symbols for logic gates are shown.

Draw **one** line to link each logic function to its standard symbol. **Not** all standard symbols will be used.

Logic function

AND

XOR

NAND

OR

Standard symbol

