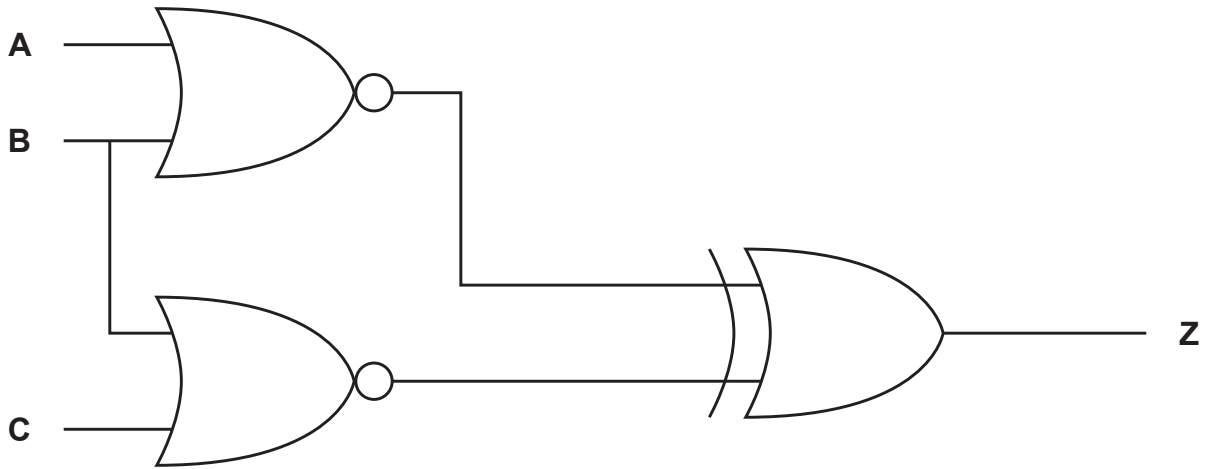


(b) Complete the truth table for this logic circuit.



A	B	C	Working space	Z
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		