

3 **Four** logic gates and **five** logic gate symbols are shown.

Draw **one** line to link each logic gate to its correct symbol. **Not** all logic gate symbols will be used.

Logic gate

AND

NAND

NOR

XOR

Logic gate symbol

