

27 A cell passes a current of 2.0 A in a circuit for 30 s . In this time, the cell transfers 120 J of energy.

What is the electromotive force (e.m.f.) of the cell?

A 0.50 V

B 1.5 V

C 2.0 V

D 8.0 V