

29 Lamps can be connected in series or in parallel to a power supply.

What is an advantage of connecting the lamps in parallel rather than in series?

- A** All of the lamps can be switched on and off using the same switch.
- B** Fewer connecting leads are needed to make the circuit.
- C** When one lamp stops working, the others may continue to work.
- D** Less power is transferred from the supply.