

27 Which circuit contains a light-dependent resistor (LDR)?

