

29 In which circuit does the lamp light?

