

- 26** A student determines the resistance of resistor R. She uses a circuit including a voltmeter and an ammeter.

Which circuit does she use?

