

7 The electromotive force (e.m.f.) of a battery is 7.5V.

(a) Define the term electromotive force.

.....  
.....  
..... [2]

(b) The battery is connected in series with a variable resistor and a  $30\Omega$  resistor. The battery is made using 1.5V cells.

(i) Draw a circuit diagram that shows all the 1.5V cells connected to produce an e.m.f. of 7.5V, the variable resistor and the  $30\Omega$  resistor.

[3]

(ii) The resistance of the variable resistor can be varied from  $0\Omega$  to a maximum resistance of  $150\Omega$ .

Using the axes in Fig. 7.1, draw a graph to show how the current in the circuit varies with the resistance of the variable resistor as it increases from  $0\Omega$  to  $150\Omega$ .

Determine and label the value of the maximum current on the y-axis.

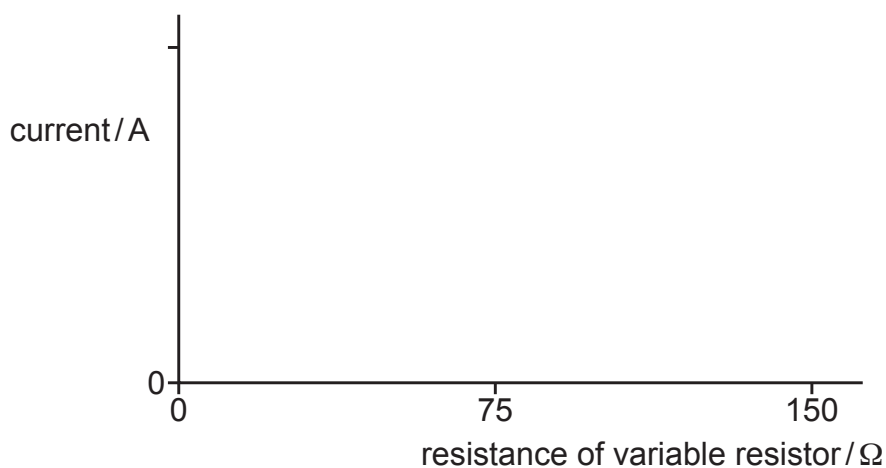


Fig. 7.1

[4]