

28 The circuits shown all include a d.c. power supply, one diode and two light-emitting diodes (LEDs).

In which circuit will both LEDs be turned on?

