

**26** Which statement about a voltmeter is correct?

**A** It has a scale which is marked in amperes (A).

**B** It must be connected in series in a circuit.

**C** It measures potential difference (p.d.).

**D** It must have three terminals.