

# Electricity

## A-Level Physics

### Electric current

An **electric current** 电流 is a flow of **charge carriers** 载流子. In a metal the carriers are negative conduction **electrons** 电子; in an **electrolyte** 电解质 they are positive and negative **ions** 离子; in a **semiconductor** 半导体 they may be electrons or "**holes**" 空穴. The **conventional current** 常规电流 direction is the way **positive** charge would flow —opposite to the real flow of electrons in a wire.

### Charge

Charge is **quantised** 量子化: the smallest free unit of charge is the **elementary charge** 基本电荷

$$e = 1.60 \times 10^{-19} \text{ C.}$$

Every free charge in this syllabus is a whole-number multiple of  $e$ . The unit of charge is the **coulomb** 库仑, C.

### Current as the rate of flow of charge

If charge  $Q$  passes a point in time  $t$ , the current is



$$I = \frac{Q}{t}, \quad Q = It.$$

Unit of current: ampere, A ( $= \text{C s}^{-1}$ ). For a changing current, the charge that has flowed in a time is the **area under** an  $I-t$  graph.

### Drift velocity equation

For a uniform conductor of cross-section area  $A$ , with  $n$  charge carriers per unit volume (the **number density** 数密度), each carrying charge  $q$ , moving with average **drift velocity** 漂移速度  $v$ :

$$I = Anvq.$$

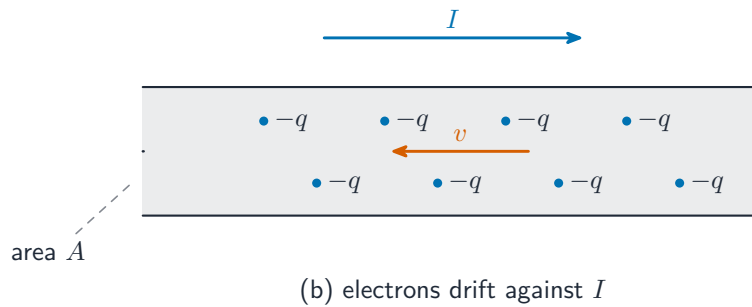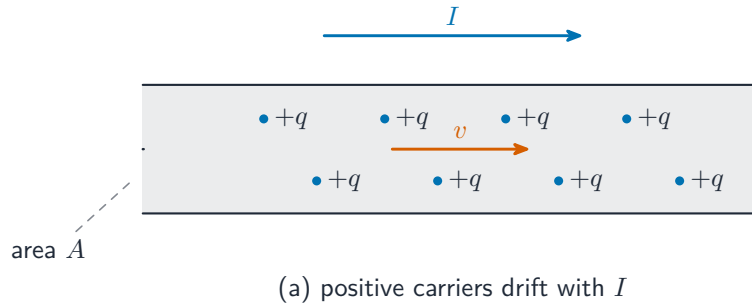

*Charge carriers drifting inside a conductor: positive carriers drift with  $I$ , electrons against it*

Use this to compare currents:

- a thinner wire (smaller  $A$ ) at the same  $I$  needs a faster drift  $v$ .
- a semiconductor has far fewer free carriers than a metal (smaller  $n$ ), so for the same  $I$  the drift velocity is much larger.
- in **series** 串联 components,  $I$  is the same everywhere, so if  $A$  stays the same but the material changes,  $nv$  changes the other way.

## Potential difference

The **potential difference** 电势差 (p.d.) across a component is the **energy** 能量 transferred per unit charge as that charge passes through it:

$$V = \frac{W}{Q}.$$

Unit: **volt** 伏特,  $V (= J C^{-1})$ .

If 1 J of electrical energy changes into other forms (thermal, light, kinetic, ...) when 1 C of charge passes through a component, the p.d. across it is 1 V.

The **electromotive force** 电动势 (e.m.f.) of a source is the energy given **per unit charge by the source**. The formula is the same as for p.d.; the difference is direction: e.m.f. is energy given **to** the charge by the source; p.d. is energy given **up** by the charge to the component.

## Electrical power



*High-voltage power lines carry electrical energy across the country.*

Image: Dmitry Makeev, CC BY-SA 4.0 (commons.wikimedia.org)

Combining  $V = W/Q$  and  $I = Q/t$ :

$$P = \frac{W}{t} = VI.$$

Using Ohm's law  $V = IR$ :

$$P = VI = I^2R = \frac{V^2}{R}.$$

Pick the form with the quantities you know. Examples:

- two heaters of equal resistance —the one with the larger current gives more **power** 功率 ( $P = I^2R$ ).
- two resistors in **parallel** 并联 across the same **voltage** 电压—the one with smaller  $R$  gives more power ( $P = V^2/R$ ).
- a kettle marked "2.4 kW, 240 V" draws  $I = P/V = 10$  A and has resistance  $R = V^2/P = 24 \Omega$ .


Energy transferred in time  $t$  is  $E = Pt$ .

## Resistance and Ohm's law

The **resistance** 电阻  $R$  of a component is

$$R = \frac{V}{I}.$$

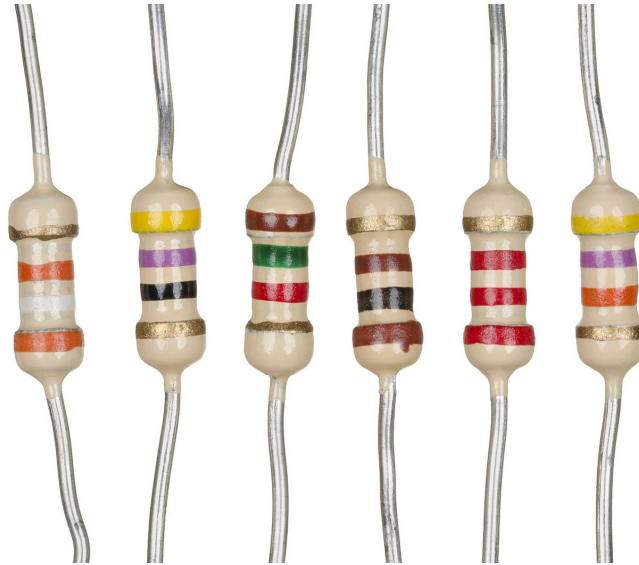Unit: **ohm** 欧姆,  $\Omega$  ( $= \text{V A}^{-1}$ ). Resistance depends on the conditions (such as temperature) when it is measured.



*Real fixed resistors —the coloured bands code the resistance in ohms*

Image: Evan-Amos, Public domain (commons.wikimedia.org)

## Ohm's law


A conductor obeys **Ohm's law** 欧姆定律 when the current through it is **proportional to the p.d.** across it, as long as the conditions (especially temperature) stay constant. For such a conductor  $R$  is constant and the  $I$ - $V$  graph is a straight line through the origin.

Ohm's law is an experimental result, not a definition. The definition  $R = V/I$  works for **any** component; only ohmic ones have constant  $R$ .

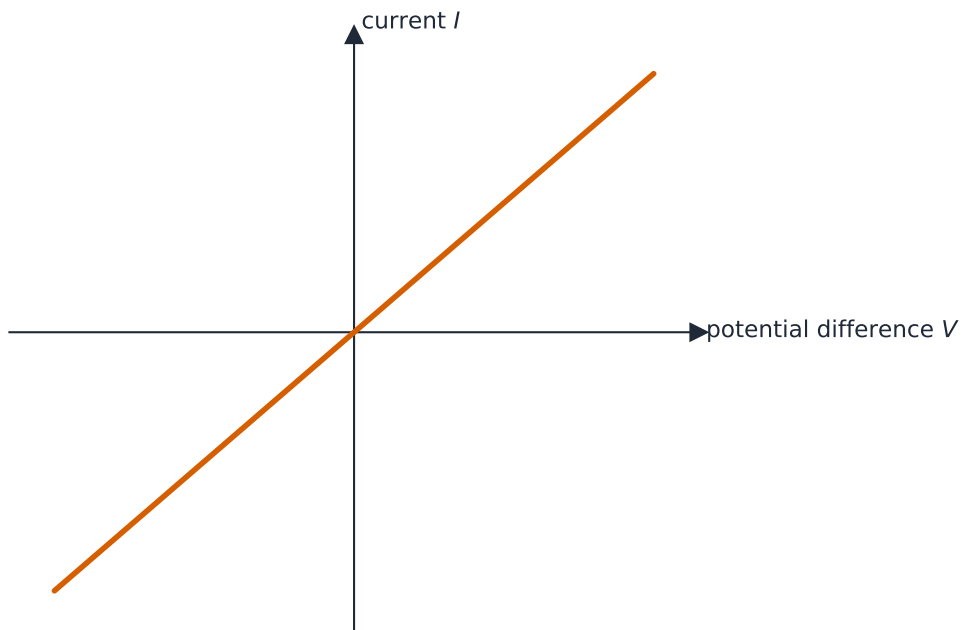
## $I$ - $V$ characteristics

You should be able to sketch these:


- **metal wire at constant temperature** —a straight line through the origin (constant  $R$ ). Reversing the p.d. drives the current the other way, giving a straight line in both directions.
- **filament lamp** 灯丝灯泡—through the origin, steep at first, then flatter as  $V$  (and  $I$ ) grow. Reason: more current heats the filament, so its resistance rises and the gradient  $1/R$  falls.
- **semiconductor diode** 二极管—almost no current for negative  $V$  or small positive  $V$ . Above a "switch-on" voltage (about 0.7 V for silicon), the current rises sharply.



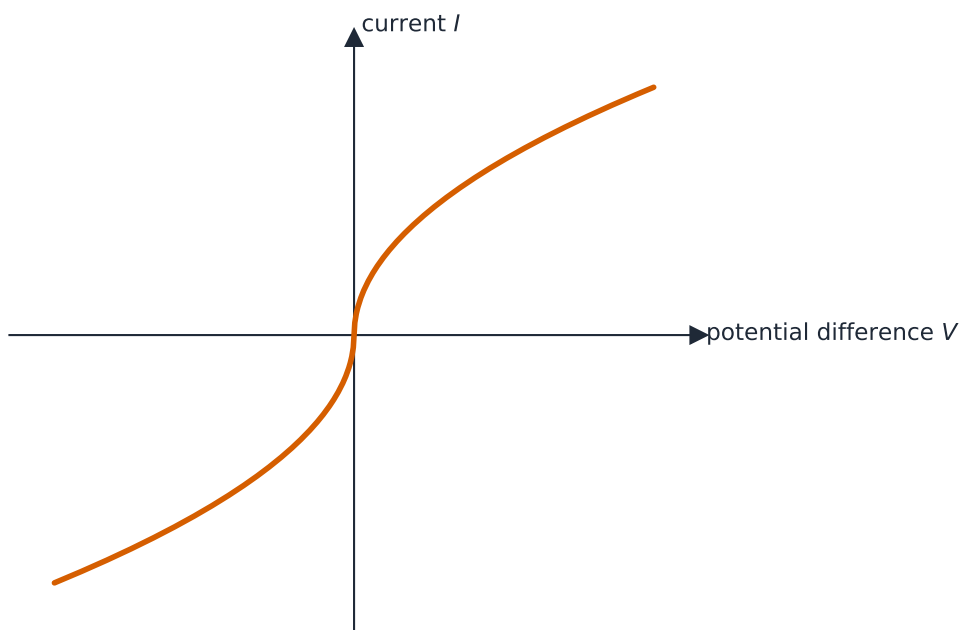*$I$ - $V$  characteristic of an ohmic conductor (metal wire at constant temperature)*



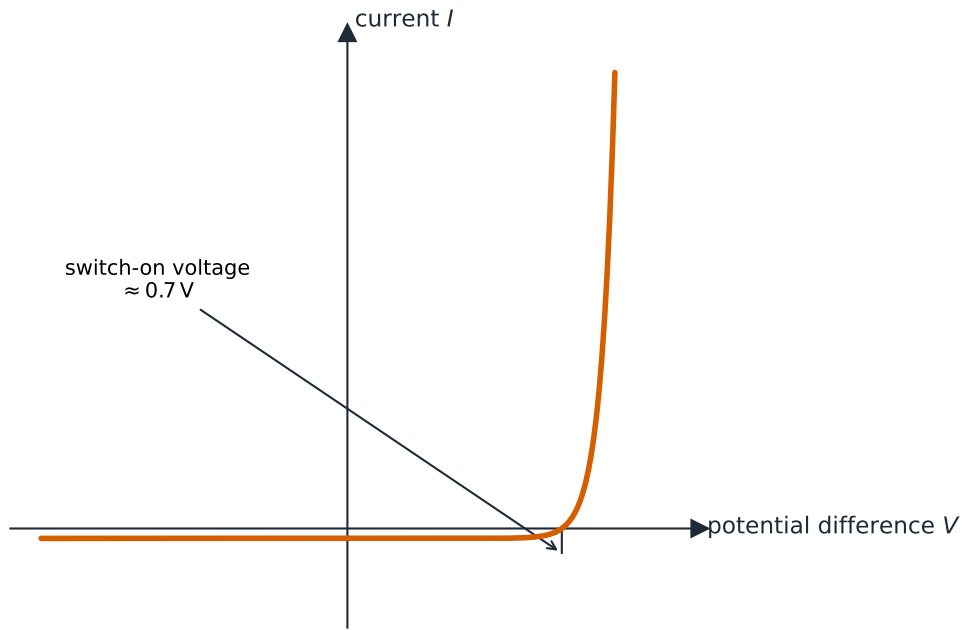*$I$ - $V$  characteristic of a filament lamp*



*I-V characteristic of a semiconductor diode*


## Resistivity

For a uniform conductor of length  $L$  and cross-section area  $A$ ,


$$R = \frac{\rho L}{A}.$$

$\rho$  is the **resistivity** 电阻率, a property of the material, with unit  $\Omega \text{ m}$ . Doubling the length doubles  $R$ ; doubling the area halves it; halving the diameter quarters the area and so makes  $R$  four times bigger.

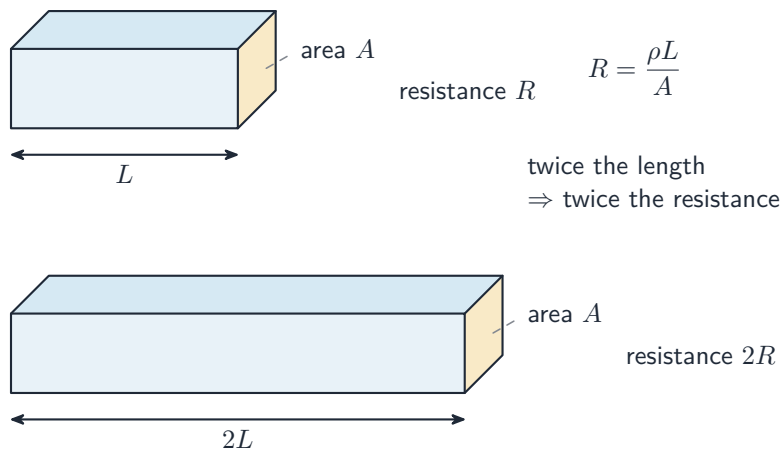Typical values: copper at room temperature  $\rho \sim 1.7 \times 10^{-8} \Omega \text{ m}$ ; an **insulator** 绝缘体  $\rho \sim 10^{15} \Omega \text{ m}$  or more.



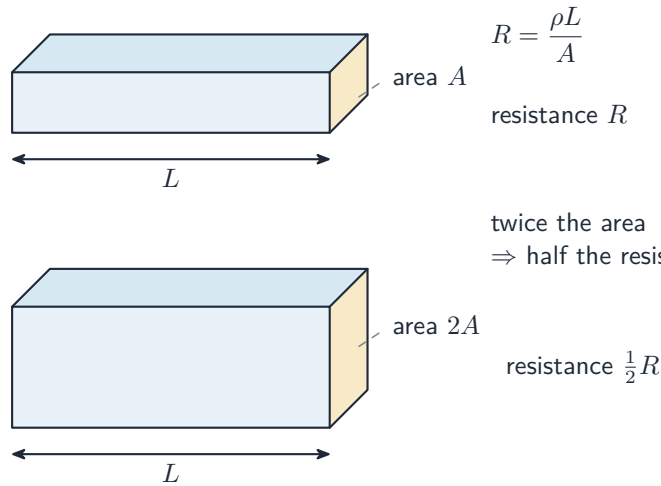*A longer conductor has more resistance — doubling  $L$  doubles  $R$*




*A wider conductor has less resistance —doubling  $A$  halves  $R$*

The resistivity of a metal **rises with temperature** (more **lattice vibration** 晶格振动 **scatters** 散射 the electrons), which is why the filament lamp's  $I$ - $V$  line curves.
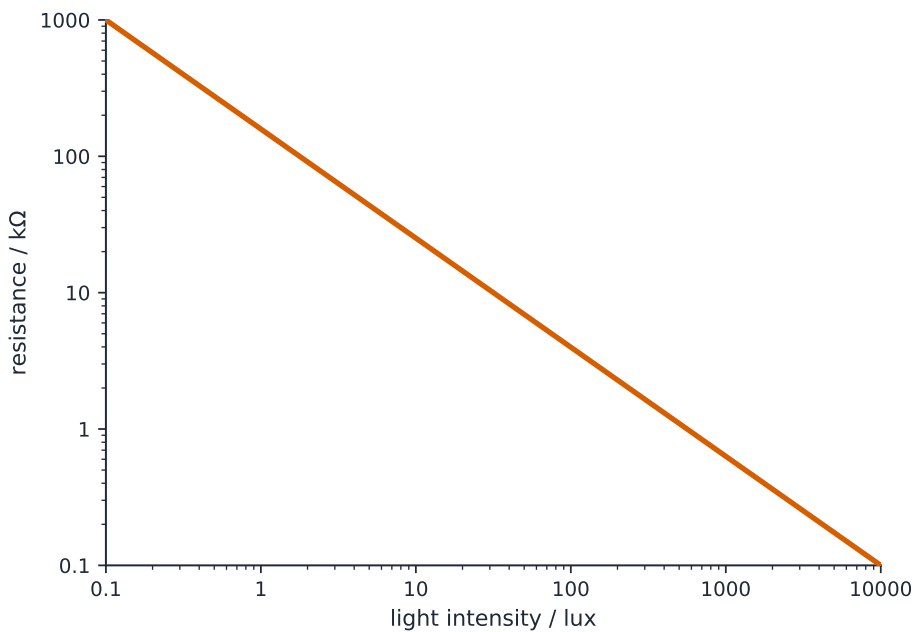
## Light-dependent resistor (LDR)


A **light-dependent resistor** 光敏电阻 (LDR) is a semiconductor whose **resistance falls as the light intensity rises**. In bright light  $R$  may be a few hundred  $\Omega$ ; in the dark it can be in the megaohms. LDRs are used in light-sensing circuits (street lamps, camera light meters). Here the **light intensity** 光强 controls the resistance.



*Resistance of an LDR decreases as light intensity increases*
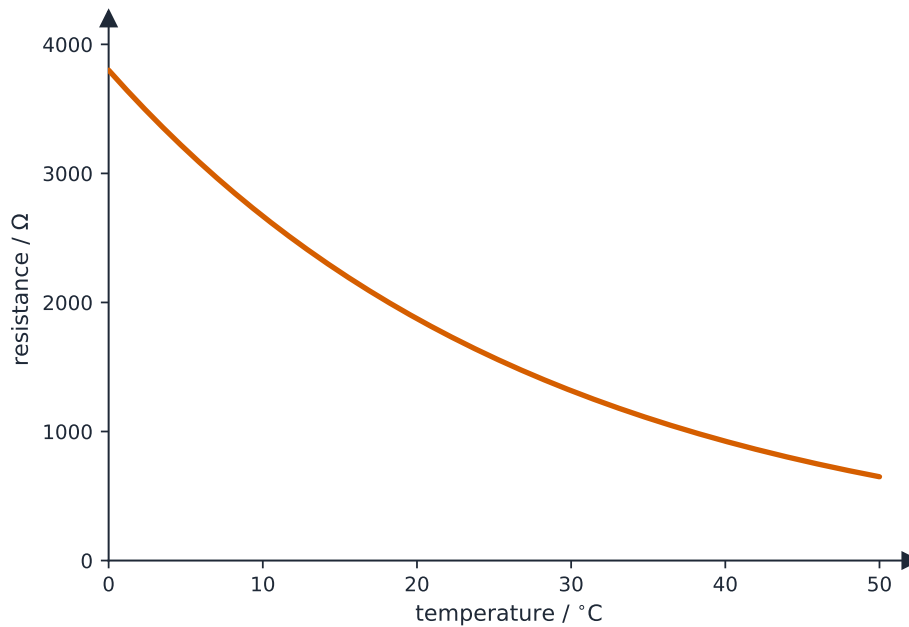
# Thermistor

In this syllabus a **thermistor** 热敏电阻 has a **negative temperature coefficient** 负温度系数: its **resistance falls as its temperature rises**. This is useful for sensing temperature —put it in a **potential divider** 分压器 and the output voltage changes with temperature.



*Resistance of a thermistor falls as temperature rises*

This is the opposite of a metal: in a semiconductor, more thermal energy frees more charge carriers, and this matters more than the extra scattering.