

11.6 Kirchhoff's Loop Rule

Name: _____ Class: _____ Date: _____

Total: 9 marks

Objective

Build the skills to answer exam questions on **Kirchhoff's loop rule**.

You must be able to:

- state **Kirchhoff's loop rule** 基尔霍夫电压定律, $\sum \Delta V = 0$ around any closed loop
- explain it as a consequence of **conservation of energy** 能量守恒
- assign consistent **sign conventions** for emf sources and resistors
- write and solve **loop equations**

1 Worked examples

Study these first. Each one shows the method for a question type used later.

■ The loop rule

Around any closed loop, $\sum \Delta V = 0$ —the rises across the emf sources balance the drops across the resistors.

■ Why it holds

A charge returning to its starting point has the **same** potential energy, so the potential changes around the loop sum to zero (conservation of energy).

■ Signs

Going around the loop: a resistor traversed with the current is a **drop** ($-IR$); an emf traversed from $-$ to $+$ is a **rise** ($+\varepsilon$).

2 Practice

2.1 State Kirchhoff's loop rule. [1]

2.2 State the conservation law the loop rule expresses. [1]

2.3 A single loop has a 10 V battery and resistors $2.0\ \Omega$ and $3.0\ \Omega$ in series. Find the

current.

[2]

3 Exam-style questions

3.1 Kirchhoff's loop rule sums the potential differences around a closed loop to

[1]

- **A** the emf
 - **B** zero
 - **C** a maximum
 - **D** infinity
-

3.2 The loop rule expresses conservation of

[1]

- **A** charge
 - **B** energy
 - **C** momentum
 - **D** mass
-

3.3 A single loop contains a 12 V battery and resistors of $3.0\ \Omega$ and $1.0\ \Omega$ in series.

(a) Write the loop equation.

[2]

(b) Find the current.

[1]

4 Go further

- work through the **11.6 Kirchhoff's Loop Rule** lesson on the **Learn** page;
- read the **Electric Circuits** section of the AP Physics C: E&M handout on the **Know** page.

Solutions

2.1 the sum of the potential differences around any closed loop is zero.

2.2 conservation of energy.

2.3 $10 = I(2.0 + 3.0) \Rightarrow I = 2.0 \text{ A}$.

3.1 B.

3.2 B.

3.3 (a) $12 = I(3.0) + I(1.0)$. (b) $I = \frac{12}{4.0} = 3.0 \text{ A}$.